 





Designing Combinational Logic Circuits

Combinational vs. Sequential Logic



Combinational


$$\text{Output} = f(\text{In})$$

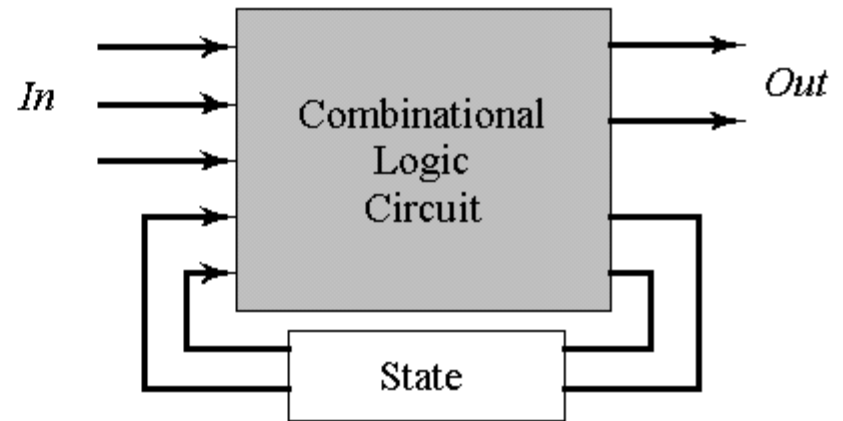

Sequential



$$\text{Output} = f(\text{In}, \text{Previous In})$$

Transistor Sizing a Complex CMOS Gate

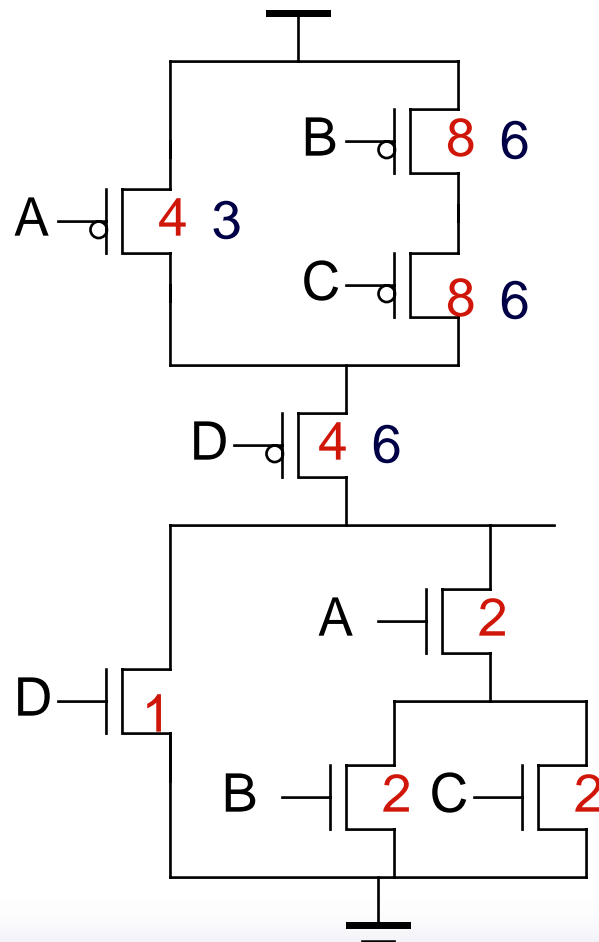

$$\text{OUT} = \overline{D + A \cdot (B + C)}$$

Fan-In Considerations

 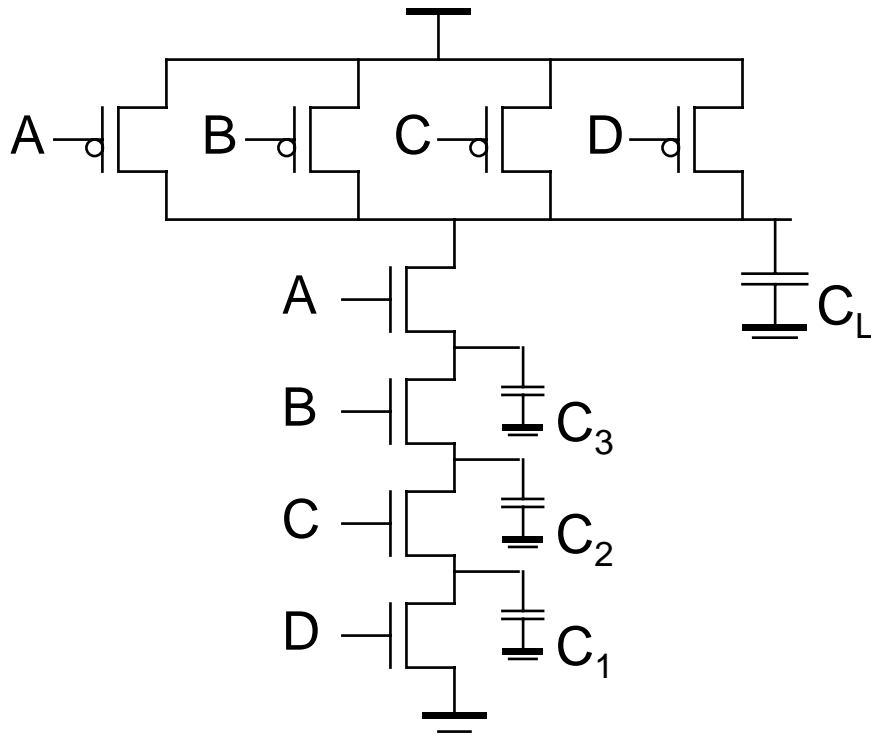

Distributed RC model
(Elmore delay), assuming all
NMOS devices of equal size


$$t_{pHL} = 0.69 R_{eqn} (C_1 + 2C_2 + 3C_3 + 4C_L)$$

Propagation delay deteriorates
rapidly as a function of fan-in –
quadratically in the worst case.

$$t_{pHL} = 0.69 [R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + (R_1 + R_2 + R_3 + R_4) C_L]$$

t_p of CMOS NAND as a Function of Fan-In

 
(Assuming a fixed fan out of one inverter)



Gates with a fan-in greater than 4 should be avoided.

linear

t_p as a Function of Fan-Out

 


All gates have the same drive current.

Slope is a function of “driving strength”

Static Complementary CMOS

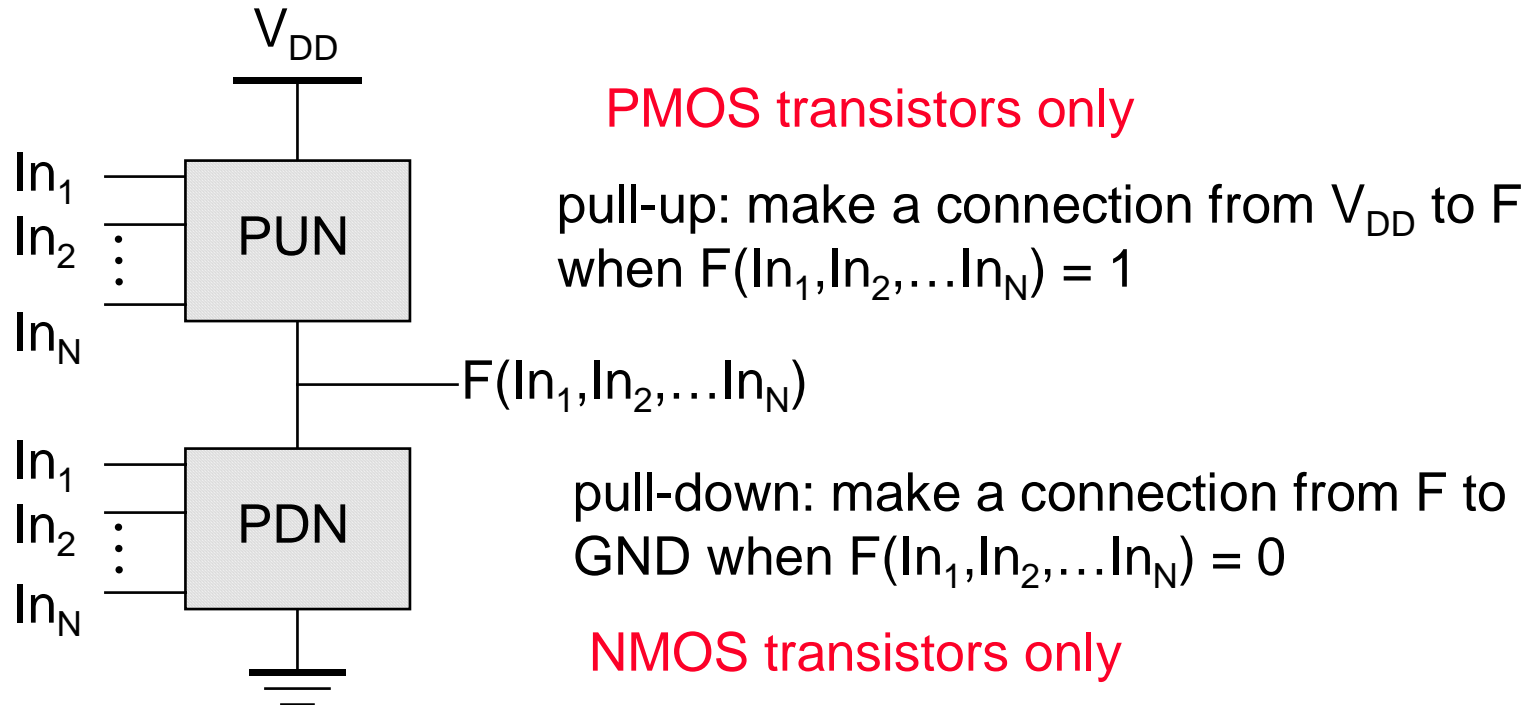- Pull-up network (PUN) and pull-down network (PDN)





PUN and PDN are **dual** logic networks



One and only one of the networks is conducting in steady state

Threshold Drops

PUN

 
 


PDN

 
 


Threshold Drops

PUN

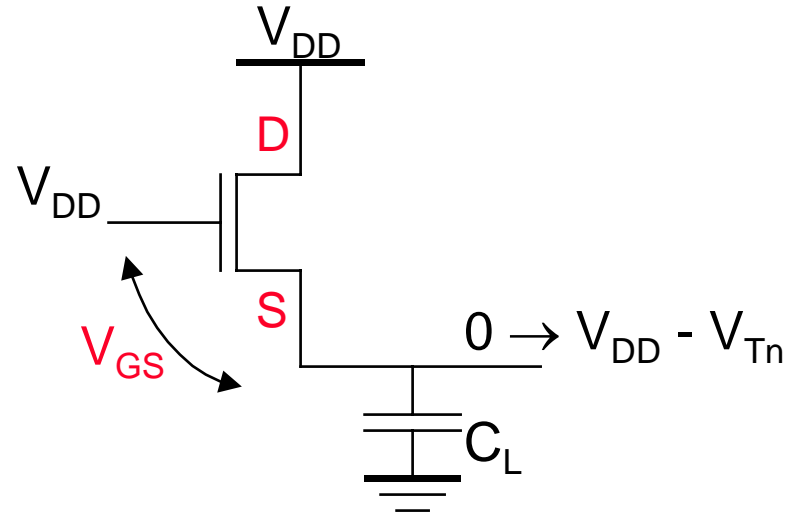 



PDN

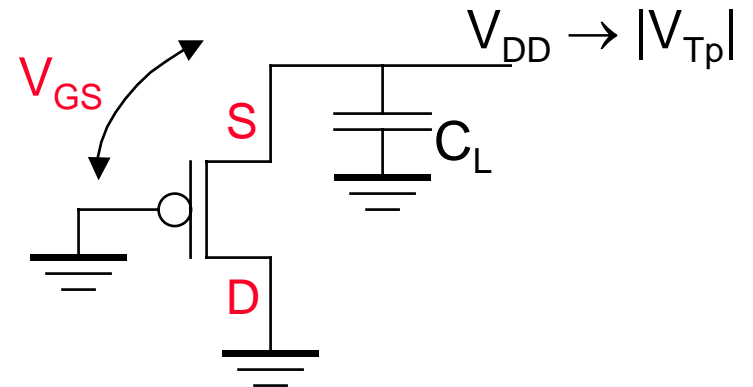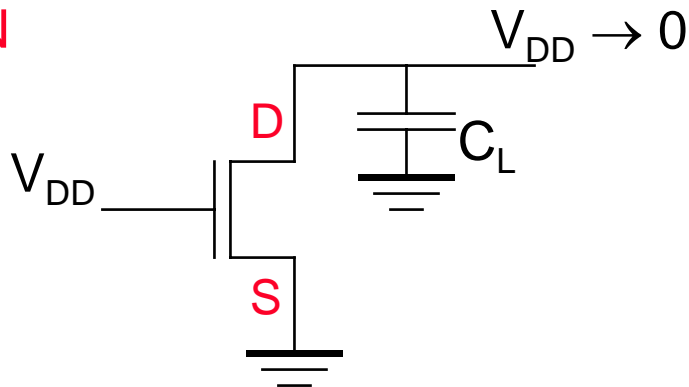

NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a switch controlled by its gate signal

 
 
NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1

PMOS Transistors in Series/Parallel Connection

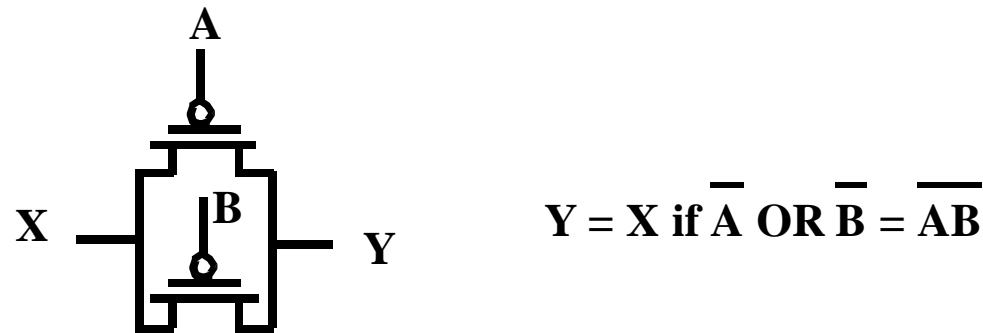 
PMOS switch closes when switch control input is low




PMOS Transistors pass a “strong” 1 but a “weak” 0

Construction of PDN

 - NMOS devices in **series** implement a NAND function



 - NMOS devices in **parallel** implement a NOR function



Dual PUN and PDN

- PUN and PDN are dual networks

λ DeMorgan's theorems

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

- λ a **parallel** connection of transistors in the PUN corresponds to a **series** connection of the PDN
- Complementary gate is naturally **inverting** (NAND, NOR, XNOR)
- Number of transistors for an N-input logic gate is **2N**


Complementary CMOS Logic Style

- **PUN is the DUAL of PDN**
(can be shown using DeMorgan's Theorem's)

$$\overline{A + B} = \bar{A}\bar{B}$$


$$\overline{\bar{A}\bar{B}} = A + B$$

 - **The complementary gate is inverting**




AND = NAND + INV


CMOS NAND

 


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 


CMOS NOR

 

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

 

Complex CMOS Gate

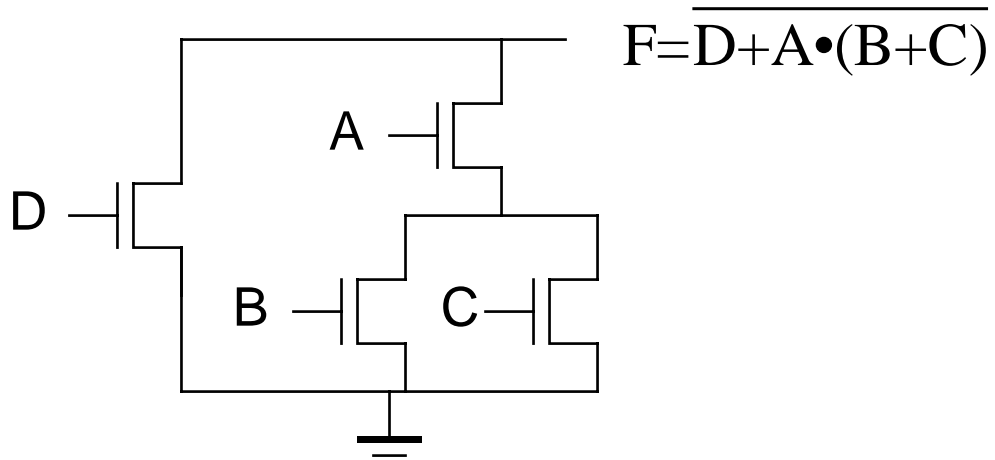

Complex CMOS Gate

